

AJAY KUMAR GARG ENGINEERING COLLEGE, GHAZIABAD
DEPARTMENT OF Electrical & Electronics Engineering

Sessional Test 2

Program: B.Tech
 Session: 2024-25
 Subject: Fundamentals of Electrical Engg.
 Max. Marks: 50

Semester: II
 Section: S11-S20
 Subject Code: BEE201
 Time: 2 Hours

OBE Remarks:

Q.No	1	2	3	4	5	6	7	8	9	10	11	12
CO No.	CO2	CO2	CO3	CO3	CO3	CO2	CO2	CO2	CO3	CO3	CO2	CO3
Bloom's Level* (L1 to L6)	L3	L2	L2	L2	L2	L3	L3	L3	L2	L2	L3	L3
Weightage CO2: 26.5						Weightage CO3: 23.5						

*Bloom's Level: L1: Remember, L2: Understand, L3: Apply, L4: Analyze, L5: Evaluate, L6: Create

Note: Answer all the sections with all the questions

Section-A

(2*5=10)

1. A resistance of 15Ω , choke coil of $0.05H$ and the capacitor of $0.03F$ are connected in series. Find the impedance of the circuit if frequency is 50 Hz .
2. Why the power in a capacitor is zero?
3. Write any 4 points of analogy between electric and magnetic circuits.
4. Why a transformer cannot be operated on DC?
5. Why the power rating of a transformer is in VA?

Section-B

(5*5=25)

6. Define form factor and peak factor, find these factors for a half wave rectified waveform.
7. A coil is connected in series with a variable capacitor C . The supply voltage is 10 V at 1000 rad/sec . The current in the circuit is maximum when $C=10\text{ microfarad}$. The current is 0.707 times the maximum current when $C=12.5\text{ microfarad}$. Find:
 - (i) Inductance and resistance of the coil.
 - (ii) Q factor of the coil at 1000 rad/sec .
 - (iii) maximum current in the circuit.
8. An impedance of $(2+j6)\Omega$ is connected in series with two impedances of $(10+j4)\Omega$ & $(12-j8)\Omega$ which are in parallel. The circuit is connected to $200\text{ V}, 50\text{ Hz}$ supply. Find:
 - (i) total circuit impedance
 - (ii) supply current & power factor
 - (iii) total power supplied by the source
9. Derive the emf equation of a transformer. Why the frequency of two sides is same?
10. Explain the working principle of transformer. Compare core and shell type transformer.

Section-C

(7.5*2=15)


11. Derive the relation between line and phase quantities for a **delta** connected balanced load. A 3-phase voltage source has a phase voltage of 120V and supplies **star** connected load having impedance $(36+j48) \Omega/\text{phase}$. Calculate:


- (a) Line voltage
- (b) line current
- (c) power factor
- (d) 3 phase power supplied to the load

12. A transformer on **no load** has core loss of 50W, draws a current of 2A and has induced emf of 230V. Determine:

- (i) no load power factor
- (ii) core loss current and magnetizing current.

Also calculate the no load circuit parameters of the transformer. Neglect winding resistance and leakage flux.

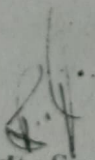
Faculty Sign

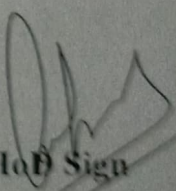
HoD Sign