

Ajay Kumar Garg Engineering College, Ghaziabad

Department of Electrical & Electronics Engineering

Pre-University Test

Course: B.Tech
 Session: 2024-25
 Subject: Fundamentals of Electrical Engg.
 Max Marks: 70

Semester: II
 Section: S11 to S20
 Sub. Code: BEE-201
 Time: 3Hrs.

OBE Remarks:

Q.No.	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17
CO No.	1	1	2	3	3	4	5	1	2	2	3	3	4	4	5	5	1
Bloom's Level	L-1	L-1	L-2	L-2	L-1	L-2	L-3	L-3	L-2	L-3	L-2	L-2	L-1	L-2	L-2	L-2	L-3
Weightage CO4: 16										Weightage CO5: 16							

Note : Answer **all** the sections.

Section-A

A. Attempt **all** the parts.

(7x2 = 14)


1. Define bilateral and unilateral element with example.
2. Differentiate between ideal voltage source and practical voltage source.
3. In a series RLC circuit, $R = 2\Omega$, $L = 2\text{mH}$, $C = 10\mu\text{F}$. Find the resonant frequency and Q-factor.
4. What is the condition for positive voltage regulation in a transformer?
5. Draw the phasor diagram of practical transformer at no load condition.
6. Define the function of commutator in DC machine.
7. What is Switch fuse unit(SFU)?

Section-B

B. Attempt **Any three**.

(3x7 = 21)

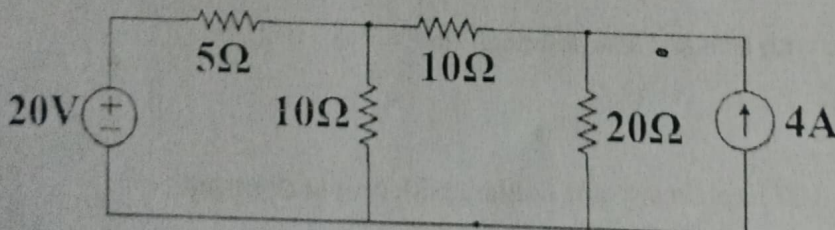8. Calculate the current across 20Ω resistor using nodal analysis in the following circuit:



9. Derive mathematically dynamic impedance (ZD) offered by RLC parallel circuit under resonance. Also, draw its phasor diagram.

- ### Section-C

(5x7 = 35)


b) Why earthing is required? Explain any one method with proper diagram.

16. Attempt any one.

- a) Name and explain the various cables and wires used in electrical system based on insulation.
- b) Classify and explain various types of batteries with their advantages and applications.

17. Attempt any one.

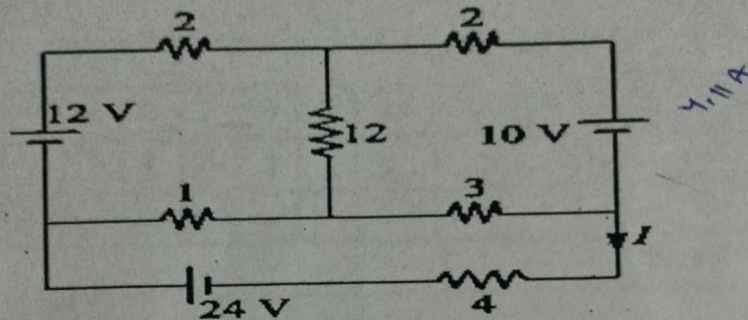- a) Determine the current in 4 ohm branch in the circuit shown below, using mesh analysis.



- b) Three impedances of $(70.7 + j 70.7)$ Ohm, $(120 + j 160)$ Ohm and $(120 + j 90)$ Ohm are connected in parallel across a 250 V supply. Determine (i) admittance of the circuit (ii) supply current and (iii) circuit power factor.

[Signature]

Faculty Sign

[Signature]

HOD Sign